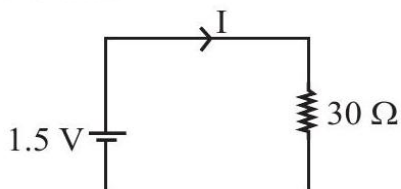


# Electricity

## Multiple Choice Questions

- 1 The charge of 150 coulomb flows through a wire in one minute. What is the electric current flowing through it?
- (a) 2.5 A
  - (c) 4.5 A
  - (b) 3.5 A
  - (d) 5.5 A

- 2 Find the current  $I$  flown in the circuit
- (a) 0.05 A
  - (b) 5 A
  - (c) 50 A
  - (d) 500 A



- 3 A current of 10 A flows through a conductor for 2 minutes. What is the amount of charge passed through the conductor?
- (a) 1200C
  - (b) 150C
  - (c) 18C
  - (d) 1.8C
- 4 A current of 10 A flows through a conductor for 2 minutes. Find the total number of electrons flowing through the conductor.
- (a)  $75 \times 10^{20}$
  - (b)  $70 \times 10^{15}$
  - (c)  $60 \times 10^{15}$
  - (d)  $11 \times 10^{12}$
- 5 A metal wire 80 cm long and  $1.00 \text{ mm}^2$  in cross-section has a resistance of 0.92ohm. It's resistivity is:
- (a) 0.000115ohmm
  - (c) 1.15ohmm
  - (b) 0.0115 ohm m
  - (d) None of these
- 6 1 Ampere is equivalent to:
- (a)  $\frac{1 \text{ coulomb}}{1 \text{ sec}}$
  - (b)  $\frac{1 \text{ volt}}{1 \text{ sec}}$
  - (c)  $\frac{1 \text{ volt meter}}{1 \text{ sec}}$
  - (d) None


7 Device used to measure electric current is:

- (a) Ammeter
- (c) Galvanometer
- (b) Voltmeter
- (d) Generator

8 Reciprocal of resistance is called:

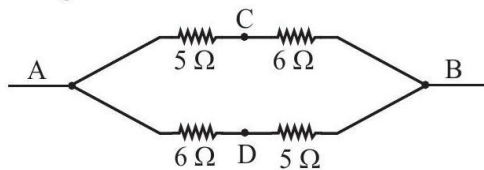- (a) Inductance
- (b) Conductance
- (c) Resistivity
- (d) None of these

9 Find the equivalent resistance between  $A$  and  $B$  of following circuit:



- (a)  $\frac{6}{2} \Omega$
- (b)  $\frac{5}{2} \Omega$
- (c)  $\frac{11}{2} \Omega$
- (d)  $\frac{1}{2} \Omega$

10 The maximum resistance which can be made using four resistors each of resistance  $\frac{1}{2} \Omega$  is


- (a)  $2 \Omega$
- (b)  $1 \Omega$
- (c)  $2.5 \Omega$
- (d)  $5 \Omega$

11 A current of 1 A is drawn by a filament of an electric bulb. Number of electrons passing through a cross section of the filament in 16 seconds would be roughly

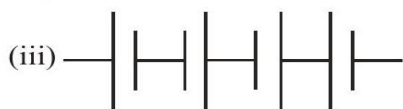- (a)  $10^{20}$
- (c)  $10^{18}$
- (b)  $10^{16}$
- (d)  $10^{23}$

12 The proper representation of series combination of cells (Figure) obtaining maximum potential is





- (a) (i)
- (b) (ii)
- (c) (iii)
- (d) (iv)

- 13 A cylindrical conductor of length  $l$  and uniform area of crosssection  $A$  has resistance  $R$ . Another conductor of length  $2l$  and resistance  $R$  of the same material has area of cross section
- (a)  $A/2$
  - (c)  $2A$
  - (b)  $3A/2$
  - (d)  $3A$
- 14 If 'i' is the current flowing through a conductor of resistance 'R' for time 't'. then the heat produced (Q) is given by
- (a)  $\frac{i^2 R}{t}$
  - (c)  $i^2 R t$
  - (b)  $\frac{i R^2}{t}$
  - (d)  $i R t^2$
- 15 An electric kettle consumes 1 kW of electric power when operated at 220 V. A fuse wire of what rating must be used for it?
- (a) 1 A
  - (b) 2 A
  - (c) 4 A
  - (d) 5 A
- 16 A cylindrical rod is reformed to twice its length with no change in its volume. If the resistance of the rod was  $R$ , the new resistance will be
- (a)  $R$
  - (b)  $2R$
  - (c)  $4R$
  - (d)  $8R$
- 17 What is the current through a 5.0ohm resistor if the voltage across it is 10 V
- (a) zero
  - (b) 0.50 A
  - (c) 2.0 A
  - (d) 5.0 A
- 18 The length of a wire is doubled and the radius is doubled. By what factor does the resistance change
- (a) 4 times as large
  - (c) unchanged

- (b) twice as large  
(d) half as large
- 19 Resistance of a metallic conductor depends on  
(a) its length  
(c) its temperature  
(b) its area of cross section  
(d) All the above
- 20 A 24 V potential difference is applied across a parallel combination of four 6ohm resistor. The current in each resistor is  
(a) 1 A  
(b) 4 A  
(c) 16 A  
(d) 36 A
- 21 Three resistances of  $2\Omega$ ,  $3\Omega$  and  $5\Omega$  are connected in parallel to a 10 V battery of negligible internal resistance. The potential difference across the  $3\Omega$  resistance will be  
(a) 2 V  
(b) 3 V  
(c) 5 V  
(d) 10 V
- 22 Two unequal resistances are connected in parallel. Which of the following statement is true  
(a) current in same in both  
(b) current is larger in higher resistance  
(c) voltage-drop is same across both  
(d) voltage-drop is lower in lower resistance
- 23 You are given  $n$  identical wires, each of resistance  $R$ . When these are connected in parallel, the equivalent resistance is  $X$ . When these will be connected in series, then the equivalent resistance will be  
(a)  $X/n^2$   
(c)  $X/n$   
(b)  $n^2X$   
(d)  $nX$
- 24 A piece of wire of resistance  $R$  is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is  $R'$ , then the ratio  $R/R'$  is  
(a)  $1/25$   
(b)  $1/5$   
(c) 5  
(d) 25
- 25 2 ampere current is flowing through a conductor from a 10 volt emf source then resistance of conductor is  
(a)  $20\Omega$   
(c)  $12\Omega$   
(b)  $5\Omega$   
(d)  $8\Omega$
- 26 Charge on an electron is  $1.6 \times 10^{-19}$  coulomb. Number of electrons passing through the wire per second on flowing of 1 ampere current through the wire will be


- (a)  $0.625 \times 10^{-19}$
- (c)  $1.6 \times 10^{-19}$
- (b)  $1.6 \times 10^{-19}$
- (d)  $0.625 \times 10^{19}$

27 20 coulomb charge is flowing in 0.5 second from a point in an electric circuit then value of electric current in amperes will be

- (a) 10
- (b) 40
- (c) 0.005
- (d) 0.05

28 In this circuit, the value of  $I_2$  is

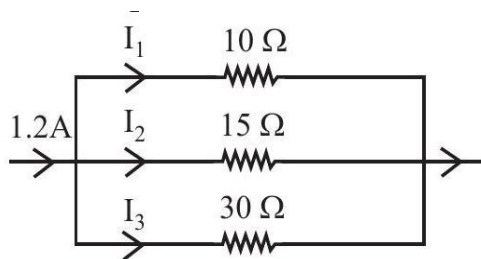- (a) 0.2 A
- (b) 0.3 A
- (c) 0.4 A
- (d) 0.6 A



29 A letter 'A' is constructed of a uniform wire of resistance 1ohm per cm. The sides of the letter are 20 cm and the cross piece in the middle is 10 cm long. The resistance between the ends of the legs will be

- (a) 32.4ohm
- (c) 26.7ohm
- (b) 28.7ohm
- (d) 24.7ohm

30 A wire of resistance R is cut into ten equal parts which are then joined in parallel. The new resistance is

- (a) 0.01R
- (b) 0.1R
- (c) 10R
- (d) 100R

31 If a wire is stretched to make its length three times, its resistance will become

- (a) three times
- (b) one-third
- (c) nine times
- (d) one-ninth


32 The resistivity of a wire depends on

- (a) length
- (b) area of cross-section
- (c) material
- (d) All the above


33 The effective resistance between the points A and B in the figure is

- (a)  $5\Omega$

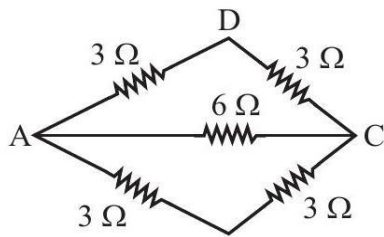
- (b)  $2\Omega$
- (c)  $3\Omega$
- (d)  $4\Omega$



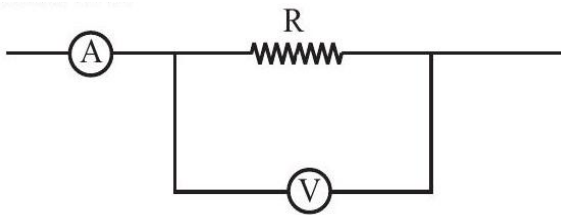- 34 In the circuits shown below the ammeter A reads 4amp. and the voltmeter V reads 20 volts. The value of the resistance  $R$  is



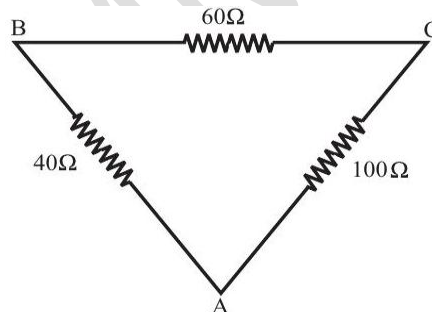- (a) slightly more than 5ohms
  - (b) slightly less than 5 ohms
  - (c) exactly 5 ohms
  - (d) None of the above
- 35 Three resistors are connected to form the sides of a triangle ABC as shown below.



The resistance of side AB is 40 ohms, of side BC 60 ohms and of side CA 100 ohms. The effective resistance between the point A and B in ohms is

- (a) 50
  - (b) 64
  - (c) 32
  - (d) 100
- 36 If one micro-amp. current is flowing in a wire, the number of electrons which pass from one end of the wire to the other end in one second is
- (a)  $6.25 \times 10^{12}$
  - (b)  $6.25 \times 10^{15}$
  - (c)  $6.25 \times 10^{18}$
  - (d)  $6.25 \times 10^{19}$

- 37 The unit for specific resistance is
- (a) ohm  $\times$  second


- (b)  $\text{ohm} \times \text{m}$
- (c) ohm
- (d)  $\text{ohm/cm}$

38 If the temperature of a conductor is increased, its resistance will

- (a) not increase
- (b) increase
- (c) decrease
- (d) change according to the whether

39 The equivalent resistance between points a and b of a network shown in the figure is given by

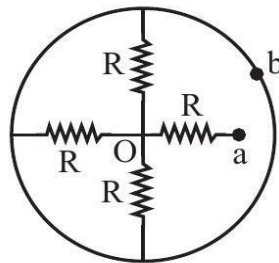- (a)  $\frac{3}{4}R$
- (b)  $\frac{4}{3}R$
- (c)  $\frac{5}{4}R$
- (d)  $\frac{4}{5}R$




40 Two wires of resistance  $R_1$  and  $R_2$  are joined in parallel. The equivalent resistance of the combination is

- (a)  $R_1 R_2 / (R_1 + R_2)$
- (b)  $(R_1 + R_2)$
- (c)  $R_1 \times R_2$
- (d)  $R_1 / R_2$

41 In the given circuit, the potential of the point E is

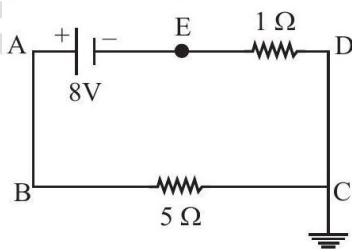- (a) Zero
- (b)  $-8 \text{ V}$
- (c)  $-4/3 \text{ V}$
- (d)  $4/3 \text{ V}$



42 The resistance of a thin wire in comparison of a thick wire of the same material

- (a) is low
- (b) is equal
- (c) depends upon the metal of the wire
- (d) is high

- 43 If the specific resistance of a wire of length  $l$  and radius  $r$  is  $k$  then resistance is  
 (a)  $k\pi r^2/l$   
 (b)  $\pi r^2/lk$   
 (c)  $kl/\pi r^2$   
 (d)  $k/lr^2$
- 44 If a charge of  $1.6 \times 10^{-19}$  coulomb flows per second through any cross section of any conductor, the current constitute will be  
 (a)  $2.56 \times 10^{-19}$  A  
 (b)  $6.25 \times 10^{-19}$  A  
 (c)  $1.6 \times 10^{-19}$  A  
 (d)  $3.2 \times 10^{-19}$  A
- 45 The number of electrons flowing per second through any cross section of wire, if it carries a current of one ampere, will be  
 (a)  $2.5 \times 10^{18}$   
 (b)  $6.25 \times 10^{18}$   
 (c)  $12.5 \times 10^{18}$   
 (d)  $5 \times 10^{18}$
- 46 The number of electron passing through a heater wire in one minute, if it carries a current of 8 ampere, will be  
 (a)  $2 \times 10^{20}$   
 (b)  $2 \times 10^{21}$   
 (c)  $3 \times 10^{20}$   
 (d)  $3 \times 10^{21}$
- 47 The heat produced in a wire of resistance ' $x$ ' when a current ' $y$ ' flow through it in time ' $z$ ' is given by  
 (a)  $x^2 \times y \times z$   
 (c)  $x \times z \times y^2$   
 (b)  $y \times z^2 \times x$   
 (d)  $y \times z \times x$
- 48 In a wire of length 4 m and diameter 6 mm, a current of 120 ampere is passed. The potential difference across the wire is found to be 18 volt. The resistance of wire will be  
 (a) 0.15ohm  
 (b) 0.25ohm  
 (c) 6.660ohm  
 (d) None of the these
- 49 The resistance of an incandescent lamp is  
 (a) greater when switched off  
 (b) smaller when switched on  
 (c) grater when switched on  
 (d) Same whether it is switched off or switched on
- 50 If resistance of a wire formed by 1. cc of copper be  $2.46\Omega$ . The diameter of wire is 0.32 mm, then the specific resistance of wire will be  
 (a)  $1.59 \times 10^{-6}$  ohm. cm  
 (b)  $2.32 \times 10^{-6}$  ohm. cm  
 (c)  $3.59 \times 10^{-6}$  ohm. cm  
 (d)  $1.59 \times 10^{-8}$  ohm. cm



- 51 A given piece of wire length  $\ell$ , cross sectional area  $A$  and resistance  $R$  is stretched uniformly to a wire of length  $2\ell$ . The new resistance will be  
(a)  $2R$   
(b)  $4R$   
(c)  $R/2$   
(d) Remains unchanged
- 52 A given piece of wire of length  $\ell$ , radius  $r$  and resistance  $R$  is stretched uniformly to a wire of radius  $(r/2)$ . The new resistances will be  
(a)  $2R$   
(b)  $4R$   
(c)  $8R$   
(d)  $16R$
- 53 There are two wires of the same length and of the same material and radial  $r$  and  $2r$ . The ratio of their specific resistance is  
(a) 1: 2  
(b) 1: 1  
(c) 1: 4  
(d) 4: 1
- 54 Specific resistance of a wire depends on the  
(a) length of the wire  
(b) area of cross-section of the wire  
(c) resistance of the wire  
(d) material of the wire
- 55 The resistance of some substances become zero at very low temperature, then these substances are called  
(a) good conductors  
(b) super conductors  
(c) bad conductors  
(d) semi conductors
- 56 The resistance of wire is  $20\Omega$ . The wire is stretched to three time its length. Then the resistance will now be  
(a)  $6.67\Omega$   
(b)  $60\Omega$   
(c)  $120\Omega$   
(d)  $180\Omega$
- 57 When the resistance of copper wire is  $0.1\Omega$  and the radius is 1 mm, then the length of the wire is (specific resistance of copper is  $3.14 \times 10^{-8}\text{ohm} \times \text{m}$ )  
(a) 10 cm  
(b) 10 m  
(c) 100 m  
(d) 100 cm
- 58 When the resistance wire is passed through a die the cross-section area decreases by 1%, the change in resistance of the wire is  
(a) 1% decrease  
(b) 1% increase  
(c) 2% decrease  
(d) 2% increase

59 The lowest resistance which can be obtained by connecting 10 resistors each of  $\frac{1}{10}$  ohm is

- (a)  $\frac{1}{250} \Omega$
- (b)  $\frac{1}{200} \Omega$
- (c)  $\frac{1}{100} \Omega$
- (d)  $\frac{1}{10} \Omega$


60 The resistance  $4R, 16R, 64R, \infty$  are connected in series, their resultant will be

- (a) 0
- (b)
- (c)  $4/3R$
- (d)  $3/4R$

61 Resistance  $R, 2R, 4R, 8R, \infty$  are connected in parallel. Their resultant resistance will be

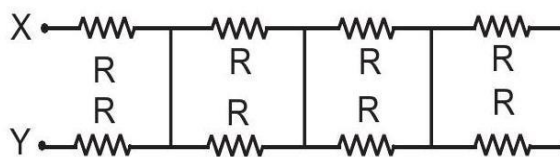
- (a)  $R$
- (b)  $R/2$
- (c) 0
- (d)  $\infty$

62 The equivalent resistance between points X and Y is



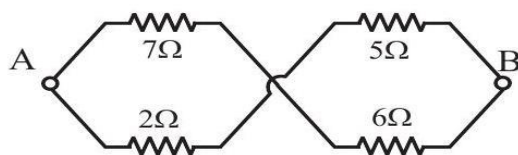- (a)  $R$
- (b)  $2R$
- (c)  $R/2$
- (d)  $4R$

63 The equivalent resistance between points A and B is



- (a)  $4\Omega$
- (b)  $4.5\Omega$
- (c)  $2\Omega$
- (d)  $20\Omega$


64 Three resistances  $4\Omega$  each of are connected in the form of an equilateral triangle. The effective resistance between two corners is

- (a)  $8\Omega$
- (b)  $12\Omega$
- (c)  $3/8\Omega$
- (d)  $8/3\Omega$

- 65 Two wires of same metal have the same length but their cross-sections area in the ratio 3: 1. They are joined in series. The resistance of the thicker wire is  $10\Omega$ . The total resistance of the combination will be  
(a)  $40\Omega$   
(b)  $40/3\Omega$   
(c)  $5/2\Omega$   
(d)  $100\Omega$
- 66 A certain piece of silver of given mass is to be made like a wire. Which of the following combination of length (L) and the area of cross-sectional (A) will lead to the smallest resistance  
(a) L and A  
(b)  $2L$  and  $A/2$   
(c)  $L/2$  and  $2A$   
(d) Any of the above, because volume of silver remains same
- 67 A certain wire has a resistance R. The resistance of another wire identical with the first except having twice of its diameter is  
(a)  $2R$   
(b)  $0.25R$   
(c)  $4R$   
(d)  $0.5R$
- 68 What length of the wire of specific resistance  $48 \times 10^{-8} \Omega - m$  is needed to make a resistance of  $4.2\Omega$  (diameter of wire =  $0.4 \text{ mm}$ )  
(a)  $4.1 \text{ m}$   
(b)  $3.1 \text{ m}$   
(c)  $2.1 \text{ m}$   
(d)  $1.1 \text{ m}$
- 69 The resistance of an ideal voltmeter is  
(a) zero  
(c) very large  
(b) very low  
(d) Infinite
- 70 Masses of 3 wires of same metal are in the ratio 1: 2: 3 and their lengths are in the ratio 3: 2: 1. The electrical resistances are in ratio  
(a) 1: 4: 9  
(b) 9: 4: 1  
(c) 1: 2: 3  
(d) 27: 6: 1
- 71 We have two wires A and B of same mass and same material. The diameter of the wire A is half of that B. If the resistance of wire A is  $24\text{ohm}$  then the resistance of wire B will be  
(a)  $12\text{ohm}$   
(c)  $1.5\text{ohm}$   
(b)  $3.0\text{ohm}$   
(d) None of the above
- 72 The electric resistance of a certain wire of iron is R. If its length and radius are both doubled, then  
(a) The resistance will be doubled and the specific resistance will be halved  
(b) The resistance will be halved and the specific resistance will remain unchanged

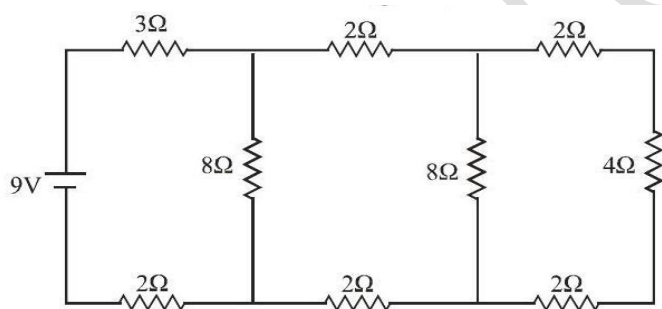- (c) The resistance will be halved and the specific resistance will be doubled
- (d) The resistance and the specific resistance, will both remain unchanged


- 73 When a wire of uniform cross-section  $a$ , length  $\ell$  and resistance  $R$  is bent into a complete circle, resistance between any two of diametrically opposite points will be
- (a)  $R/4$
  - (b)  $R/8$
  - (c)  $4R$
  - (d)  $R/2$
- 74 A solenoid is at potential difference 60 V and current flows through it is 15 ampere, then the resistance of coil will be
- (a)  $4\Omega$
  - (b)  $8\Omega$
  - (c)  $0.25\Omega$
  - (d)  $2\Omega$
- 75 A strip of copper and another of germanium are cooled from room temperature to 80 K. The resistance of
- (a) Each of these increases
  - (b) Each of these decreases
  - (c) Copper strip increases and that of germanium decreases
  - (d) Copper strip decreases and that of germanium increases
- 76 In the circuit shown in the figure, the current through



- (a) the  $3\Omega$  resistor is 0.50 A
  - (b) the  $3\Omega$  resistor is 0.25 A
  - (c) the  $4\Omega$  resistor is 0.50 A
  - (d) the  $4\Omega$  resistor is 0.25 A
- 77 Two electric lamps each of 100 watts 220 V are connected in series to a supply of 220 volts. The power consumed would be -
- (a) 100 watts
  - (b) 25 watts
  - (c) 200 watts
  - (d) 50 watts
- 78 If it takes 8 minutes to boil a quantity of water electrically, how long will it take to boil the same quantity of water using the same heating coil but with the current doubled
- (a) 32 minutes
  - (b) 16 minutes

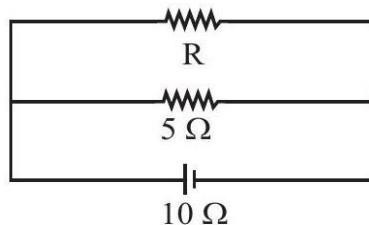
- (c) 4 minutes
- (d) 2 minutes

- 79 An electric bulb is filled with
- (a) hydrogen
  - (c) ammonia
  - (b) oxygen and hydrogen
  - (d) nitrogen and argon
- 80 When current is passed through an electric bulb, its filament glows, but the wire leading current to the bulb does not glow because
- (a) less current flows in the leading wire as compared to that in the filament
  - (b) the leading wire has more resistance than the filament
  - (c) the leading wire has less resistance than the filament
  - (d) filament has coating of fluorescent material over it
- 81 Which of the following terms does not represent electrical power in a circuit?
- (a)  $I^2 R$
  - (b)  $IR^2$
  - (c)  $VI$
  - (d)  $V^2/R$
- 82 The power dissipated in the circuit shown in the figure is 30 watts. The value of  $R$  is
- (a)  $20\Omega$
  - (b)  $15\Omega$
  - (c)  $10\Omega$
  - (d)  $30\Omega$




- 83 The filament of an electric bulb is of tungsten because
- (a) Its resistance is negligible
  - (b) It is cheaper
  - (c) Its melting point is high
  - (d) Filament is easily made
- 84 When the current passes through the filament, it gets heated to incandescence and give light while the connecting wires are not heated because
- (a) The connecting wires are good conductor of heat while the filament is bad conductor
  - (b) The connecting wires are of low resistance while the filament is of high resistance
  - (c) The density of connecting wires is less than that of the filament
  - (d) The connecting wires are bad conductor of heat while the filament is good conductor
- 85 Which one of the following heater element is used in electric press
- (a) copper wire
  - (b) nichrome wire
  - (c) lead wire
  - (d) iron wire

- 86 What should be the characteristic of fuse wire?  
 (a) High melting point, high specific resistance  
 (b) Low melting point, low specific resistance  
 (c) High melting point, low specific resistance  
 (d) Low melting point, high specific resistance
- 87 The heating element of an electric heater should be made with a material, which should have  
 (a) high specific resistance and high melting point  
 (b) high specific resistance and low melting point  
 (c) low specific resistance and low melting point  
 (d) low specific resistance and high melting point
- 88 Resistance of conductor is doubled keeping the potential difference across it constant. The rate of generation of heat will  
 (a) become one fourth  
 (b) be halved  
 (c) be doubled  
 (d) become four times
- 89 A current  $I$  passes through a wire of length  $l$ , radius  $r$  and resistivity  $\rho$ . The rate of heat generated is  
 (a)  $\frac{I^2 \rho l}{r}$   
 (b)  $\frac{I^2 \rho l}{\pi r^2}$   
 (c)  $\frac{I^2 \rho l}{\pi r}$   
 (d) none of these
- 90 The resistance  $R_1$  and  $R_2$  are joined in parallel and a current is passed so that the amount of heat liberated is  $H_1$  and  $H_2$  respectively. The ratio  $H_1/H_2$  has the value  
 (a)  $R_2/R_1$   
 (b)  $R_1/R_2$   
 (c)  $R_1^2/R_2^2$   
 (d)  $R_2^2/R_1^2$
- 91 Power dissipated across the  $8\Omega$  resistor in the circuit shown here is 2 watt. The power dissipated in watt units across the  $3\Omega$  resistor is  
 (a) 1.0  
 (b) 0.5  
 (c) 3.0  
 (d) 2.0

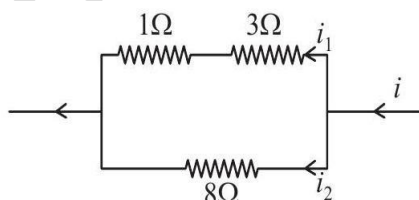

- 92 In house electrical circuits the fuse wire for safety should be of  
 (a) High resistance - high melting point  
 (b) Low resistance - high melting point  
 (c) Low resistance - low melting point  
 (d) High resistance - low melting point

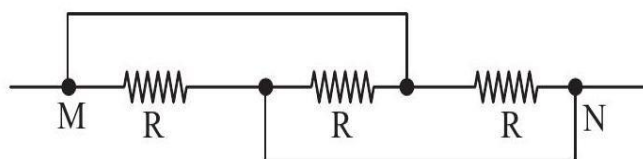93 What is the equivalent resistance of the following arrangement between M and N



- (a)  $R/2$
- (b)  $R/3$
- (c)  $R/4$
- (d)  $R/6$


94 If a wire of resistance  $1\Omega$  is stretched to double its length, then resistance will be

- (a)  $\frac{1}{2}\Omega$
- (b)  $2\Omega$
- (c)  $\frac{1}{4}\Omega$
- (d)  $4\Omega$

95 Across a metallic conductor of non-uniform cross section a constant potential difference is applied. The quantity which remains constant along the conductor is:

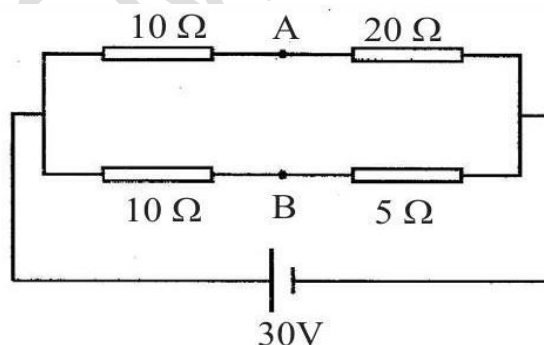- (a) current
- (b) drift velocity
- (c) electric field
- (d) current density

96 In the circuit diagram shown below,  $V_A$  and  $V_B$  are the potentials at points A and B respectively. Then,  $V_A - V_B$  is




- (a)  $-10\text{ V}$
- (b)  $-20\text{ V}$
- (c)  $0\text{ V}$
- (d)  $10\text{ V}$

97 The diameter of a wire is reduced to one-fifth of its original value by stretching it. If its initial resistance is  $R$ , what would be its resistance after reduction of the diameter?

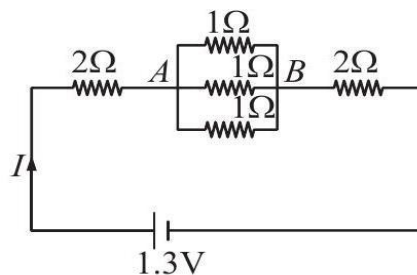- (a)  $\frac{R}{625}$
- (b)  $\frac{R}{25}$
- (c)  $25R$
- (d)  $625R$


- 98 A heater coil is cut into two equal parts and only one part is used in the heater, the heat generated now will be  
 (a) doubled  
 (b) four times  
 (c) one fourth  
 (d) halved
- 99 The resistance of a wire is  $R$ . After melting it is remoulded such that its area of cross section becomes  $n$  times its initial area of cross section. Its new resistance will be  
 (a)  $nR$   
 (b)  $\frac{R}{n}$   
 (c)  $n^2R$   
 (d)  $\frac{R}{n^2}$
- 100 The resistance of a wire is ' $R$ ' ohm. If it is melted and stretched to ' $n$ ' times its original length, its new resistance will be :  
 (a)  $\frac{R}{n}$   
 (b)  $n^2R$   
 (c)  $\frac{R}{n^2}$   
 (d)  $nR$
- 101 Three electric bulbs of rating  $40\text{ W} - 200\text{ V}$ ;  $50\text{ W} - 200\text{ V}$  and  $100\text{ W} - 200\text{ V}$  are connected in series to a  $600\text{ V}$  supply. What is likely to happen as the supply is switched on?  
 (a) Only  $50\text{ W}$  bulb will fuse  
 (b) Both  $40\text{ W}$  and  $50\text{ W}$  bulbs will fuse.  
 (c) All the three bulbs will emit light with their rated powers.  
 (d)  $100\text{ W}$  bulb will emit light of maximum intensity.
- 102 In the circuit given, the ratio of work done by the battery to maintain the current between point A and B to the work done for the whole circuit is



- (a)  $\frac{1}{117}$   
 (b)  $\frac{1}{13}$   
 (c)  $\frac{1}{12}$   
 (d) 1
- 103 What is the current supplied by the battery in the circuit shown below? Each resistance used in circuit is of  $1\text{ k}\Omega$  and potential difference  $V_{AB} = 8\text{ V}$   
 (a)  $64\text{ mA}$   
 (b)  $15\text{ mA}$




- (c) 9.87 mA  
(d) 1 mA

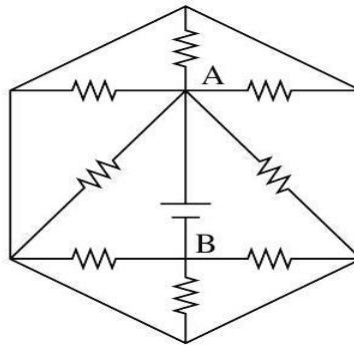

104 A wire of resistance  $R$  is bent to form a square ABCD as shown in the figure. The effective resistance between E and C is: (E is mid-point of arm CD)

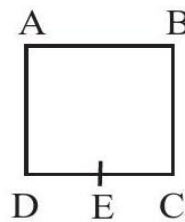
- (a)  $R$   
(b)  $\frac{7}{64} R$   
(c)  $\frac{3}{4} R$   
(d)  $\frac{1}{16} R$



105 Which of the following acts as a circuit protection device?

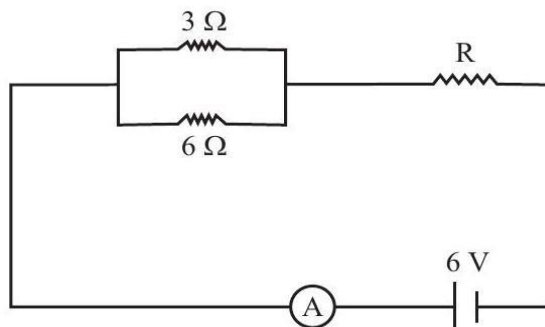
- (a) conductor  
(b) inductor  
(c) switch  
(d) fuse

106 If the ammeter in the given circuit reads 2 A, What is the value of resistance  $R$  (the resistance of ammeter is negligible).



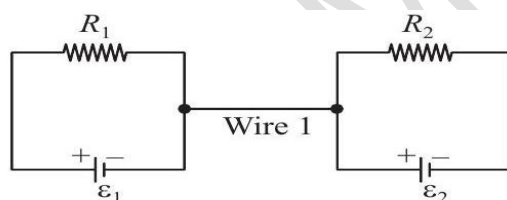- (a)  $1\Omega$   
(b)  $2\Omega$   
(c)  $3\Omega$   
(d)  $4\Omega$

- 107 A circuit to verify Ohm's law uses ammeter and voltmeter in series or parallel connected correctly to the resistor. In the circuit :
- ammeter is always used in parallel and voltmeter is series
  - Both ammeter and voltmeter must be connected in parallel
  - ammeter is always connected in series and voltmeter in parallel
  - Both, ammeter and voltmeter must be connected in series
- 108 An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be
- 100 W
  - 75 W
  - 50 W
  - 25 W
- 109 From a power station, the power is transmitted at a very high voltage because -
- it is generated only at high voltage
  - it is cheaper to produce electricity at high voltage
  - electricity at high voltage is less dangerous
  - there is less loss of energy in transmission at high voltage
- 110 Two electric bulbs rated  $P_1$  watt  $V$  volts and  $P_2$  watt  $V$  volts are connected in parallel and applied across  $V$  volts. The total power (in watts) will be
- $P_1 + P_2$
  - $\sqrt{P_1 P_2}$
  - $\frac{P_1 P_2}{P_1 + P_2}$
  - $\frac{P_1 + P_2}{P_1 P_2}$
- 111 In the circuit, wire 1 is of negligible resistance. Then,




- current will flow through wire 1 , if  $\varepsilon_1 \neq \varepsilon_2$
- current will flow through wire 1 , if  $\frac{\varepsilon_1}{R_1} \neq \frac{\varepsilon_2}{R_2}$
- current will flow through wire 1 , if

$$\frac{\varepsilon_1 + \varepsilon_2}{(R_1 + R_2)} \neq \frac{\varepsilon_1 - \varepsilon_2}{(R_1 - R_2)}$$

- no current will flow through wire 1

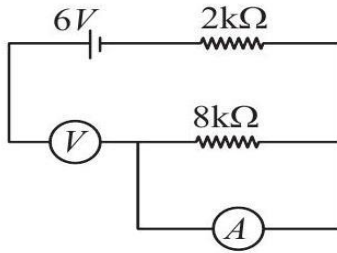- 112 In the circuit shown below, a student performing Ohm's law experiment accidentally puts the voltmeter and the ammeter as shown in the circuit below. The reading in the voltmeter will be close to
- 0 V
  - 4.8 V
  - 6.0 V
  - 1.2 V



- 113 A student in a town in India, where the price per unit (1 unit = 1 kW – hr) of electricity is ₹5.00, purchases a 1kVA UPS (uninterrupted power supply) battery. A day before the exam, 10 friends arrive to the student's home with their laptops and all connect their laptops to the UPS. Assume that each laptop has a constant power requirement of 90 W. Consider the following statements

I All the 10 laptops can be powered by the UPS if connected directly.

II All the 10 laptops can be powered if connected using an extension box with a 3 A fuse.

III If all the 10 friends use the laptop for 5 hours, then the cost of the consumed electricity is about ₹22.50.

Select the correct option with the true statements.

(a) I only

(b) I and II only

(c) I and III only

(d) II and III only

- 114 A copper wire is stretched to make it 0.5% longer. The percentage change in its electrical resistance if its volume remains unchanged is:

(a) 2.0%

(b) 2.5%

(c) 1.0%

(d) 0.5%

- 115 Six similar bulbs are connected as shown in the figure with a DC source of emf  $E$ , and zero internal resistance.


The ratio of power consumption by the bulbs when (i) all are glowing and (ii) in the situation when two from section A and one from section B are glowing, will be:

(a) 4: 9

(b) 9: 4

(c) 1: 2

(d) 2: 1

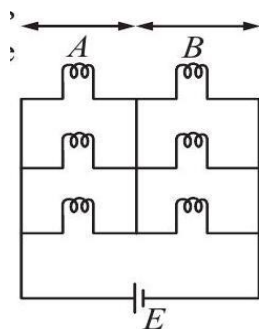

## Case/Passage Based Questions

### Case/Passage - 1

Two tungsten lamps with resistances  $R_1$  and  $R_2$  respectively at full incandescence are connected first in parallel and then in series, in a lighting circuit of negligible internal resistance. It is given that:  $R_1 > R_2$ .

- 116 Which lamp will glow more brightly when they are connected in parallel?  
 (a) Bulb having lower resistance  
 (b) Bulb having higher resistance  
 (c) Both the bulbs  
 (d) None of the two bulbs
- 117 If the lamp of resistance  $R_1$  now burns out, how will the illumination produced change?  
 (a) Net illumination will increase  
 (b) Net illumination will decrease  
 (c) Net illumination will remain same  
 (d) Net illumination will reduced to zero
- 118 Which lamp will glow more brightly when they are connected in series?  
 (a) Bulb having lower resistance  
 (b) Bulb having higher resistance  
 (c) Both the bulbs  
 (d) None of the two bulbs
- 119 If the lamp of resistance  $R_2$  now burns out and the lamp of resistance  $R_1$  alone is plugged in, will the illumination increase or decrease?  
 (a) Illumination will remain same  
 (b) Illumination will increase  
 (c) Illumination will decrease  
 (d) None
- 120 Would physically bending a supply wire cause any change in the illumination?  
 (a) Illumination will remain same  
 (b) Illumination will increase  
 (c) Illumination will decrease  
 (d) It is not possible to predict from the given datas

### Case/Passage - 2

The rate at which electric energy is dissipated or consumed in an electric circuit. This is termed as electric power,

$$P = IV, \text{ According to Ohm's law } V = IR$$

We can express the power dissipated in the alternative forms

$$P = I^2 R = \frac{V^2}{R}$$

If 100 W – 220 V is written on the bulb then it means that the bulb will consume 100 joule in one second if used at the potential difference of 220 volts. The value of electricity consumed in houses is decided on the basis of the total electric energy used. Electric power tells us about the electric energy used per second not the total electric energy.

121 The total energy used in a circuit = power of the electric circuit  $\times$  time. 121. Which of the following terms does not represent electrical power in a circuit?

- (a)  $I^2 R$
- (b)  $IR^2$
- (c)  $VI$
- (d)  $V^2/R$

122 An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be-

- (a) 100 W
- (b) 75 W
- (c) 50 W
- (d) 25 W

123 Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then in parallel in an electric circuit. The ratio of heat produced in series and in parallel combinations would be-

- (a) 1: 2
- (b) 2: 1
- (c) 1: 4
- (d) 4: 1

124 In an electrical circuit three incandescent bulbs. A, B and C of rating 40 W, 60 W and 100 W, respectively are connected in parallel to an electric source. Which of the following is likely to happen regarding their brightness?


- (a) Brightness of all the bulbs will be the same
- (b) Brightness of bulb A will be the maximum
- (c) Brightness of bulb B will be more than that of A
- (d) Brightness of bulb C will be less than that of B

125 In an electrical circuit, two resistors of  $2\Omega$  and  $4\Omega$  respectively are connected in series to a 6 V battery. The heat dissipated by the  $4\Omega$  resistor in 5 s will be

- (a) 5 J
- (b) 10 J
- (c) 20 J
- (d) 30 J
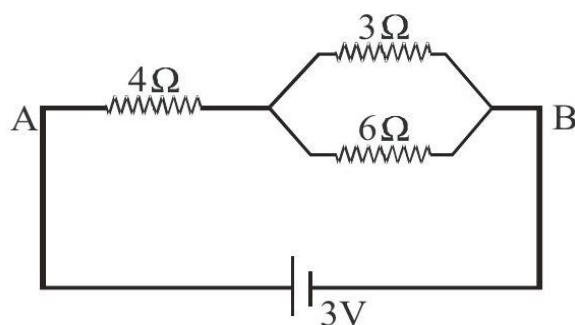
### Case/Passage - 3

Answer the following questions based on the given circuit.



126 The potential drop across the  $3\Omega$  resistor is

- (a) 1 V
- (b) 1.5 V
- (c) 2 V
- (d) 3 V

127 The equivalent resistance between points A and B is


- (a)  $7\Omega$
- (b)  $6\Omega$
- (c)  $13\Omega$
- (d)  $5\Omega$

128. The current flowing through in the given circuit is

- (a) 0.5 A
- (b) 1.5 A
- (c) 6 A
- (d) 3 A
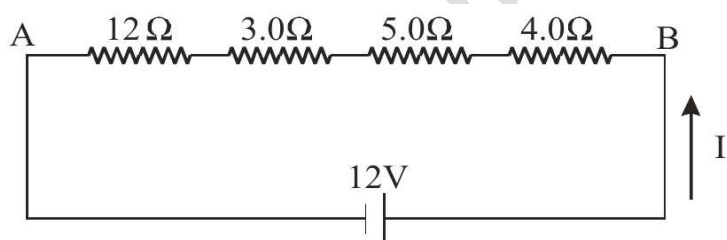
#### Case/Passage - 4

Answer the following questions based on the given circuit.



129 The equivalent resistance between points A and B, is

- (a)  $12\Omega$
- (b)  $36\Omega$
- (c)  $32\Omega$
- (d)  $24\Omega$

130 The current through each resistor is

- (a) 1 A
- (b) 2.3 A
- (c) 0.5 A
- (d) 0.75 A


131 The potential drop across the  $12\Omega$  resistor is

- (a) 12 V

- (b) 6 V
- (c) 8 V
- (d) 0.5 V
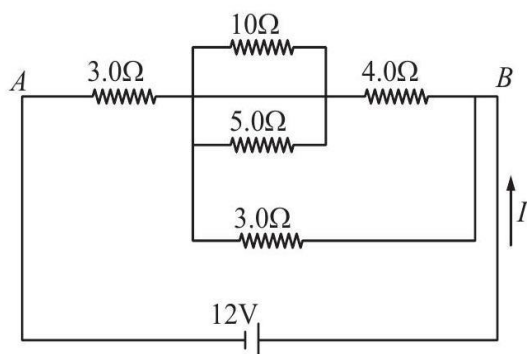
### Case/Passage - 5

Answer the following questions based on the given circuit.



132 The equivalent resistance between points A and B

- (a)  $6.2\Omega$
- (b)  $5.1\Omega$
- (c)  $13.33\Omega$
- (d)  $1.33\Omega$

133 The current through the battery is


- (a) 2.33 A
- (b) 3.12 A
- (c) 4.16 A
- (d) 5.19 A

134 The current through the  $4.0\Omega$  resistor is

- (a) 5.6 A
- (b) 0.98 A
- (c) 0.35 A
- (d) 0.68 A
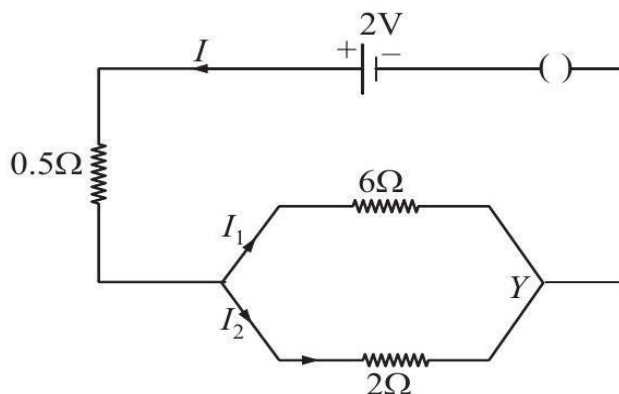
### Case/Passage - 6

Answer the following questions based on the given circuit.



- 135 The total resistance of the circuit is  
(a)  $2\Omega$   
(b)  $4\Omega$   
(c)  $1.5\Omega$   
(d)  $0.5\Omega$
- 136 The current flowing through  $0.5\Omega$  resistor is  
(a) 1 A  
(b) 1.5 A  
(c) 3 A  
(d) 2.5 A
- 137 The current flowing through  $6\Omega$  resistor is  
(a) 0.50 A  
(b) 0.75 A  
(c) 0.80 A  
(d) 0.25

## Assertion & Reason

**DIRECTIONS:** Each of these questions contains an assertion followed by reason. Read them carefully and answer the question on the basis of following options. You have to select the one that best describes the two statements.

- (a) If both Assertion and Reason are correct and Reason is the correct explanation of Assertion.  
(b) If both Assertion and Reason are correct, but Reason is not the correct explanation of Assertion.  
(c) If Assertion is correct but Reason is incorrect.  
(d) If Assertion is incorrect but Reason is correct.

138 Assertion : Fuse wire must have high resistance and low melting point.

Reason : Fuse is used for very small current flow only.

139 Assertion : Alloys are commonly used in electrical heating devices like electric iron and heater.

Reason : Resistivity of an alloy is generally higher than that of its constituent metals but the alloys have low melting points than their constituent metals.

140 Assertion : In a simple battery circuit, the point of lowest potential is negative terminal of the battery.


Reason : The current flows towards the point of higher potential as it flows in such a circuit from the negative to positive terminal.

141 Assertion : The equation  $V = Ri$  can be applied to those conducting devices which do not obey Ohm's law.

Reason :  $V = Ri$  is a statement of Ohm's law.

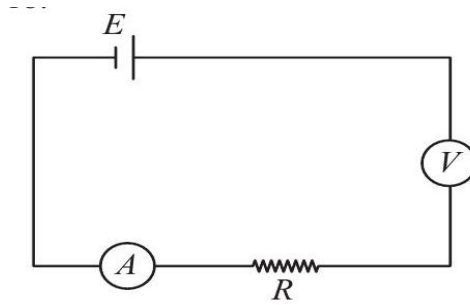142 Assertion : All electric devices shown in the circuit are ideal. The reading of each of ammeter (A) and voltmeter (V) is zero.





Reason : An ideal voltmeter draws almost no current due to very large resistance, and hence (A) will read zero.

143 Assertion : If  $\rho_1$  and  $\rho_2$  be the resistivities of the materials of two resistors of resistances  $R_1$  and  $R_2$  respectively and  $R_1 > R_2$ , then  $\rho_1 > \rho_2$ .

Reason : The resistance  $R = \rho \frac{\ell}{A} \Rightarrow \rho_1 > \rho_2$  if  $R_1 > R_2$

144 Assertion : Insulators do not allow flow of current through themselves.

Reason : They have no free-charge carriers.

145 Assertion : Positive charge inside the cell always goes from positive terminal to the negative terminal.

Reason : Positive charge inside the cell may go from negative terminal to the positive terminal.

146 Assertion : Wire A is thin in comparison to wire B of same material and same length then resistance of wire A is greater than resistance of wire B.

Reason : Resistivity of wire A is greater than resistivity of wire B.

147 Assertion : Resistivity of material may change with temperature.

Reason : Resistivity is a material property & independent on temperature.

148 Assertion : When current through a bulb decreases by 0.5%, the glow of bulb decreases by 1%.

Reason : Glow (Power) which is directly proportional to square of current.

149 Assertion : Long distance power transmission is done at high voltage.

Reason : At high voltage supply power losses are less.

150 Assertion : Resistance of 50 W bulb is greater than that of 100 W

Reason : Resistance of bulb is inversely proportional to rated power.

151 Assertion : A resistor of resistance R is connected to an ideal battery. If the value of R is decreased, the power dissipated in the circuit will increase.

Reason : The power dissipated in the circuit is directly proportional to the resistance of the circuit.