

M T W T F S S  
Page No. 38  
Date: / /  
YOUVA

3. Differentiate between conductors & insulators.

| Ans: | Conductors                                                                | Insulators                                                                  |
|------|---------------------------------------------------------------------------|-----------------------------------------------------------------------------|
| *    | Those substances which have very low resistance are called as conductors. | Those substances which have extremely high resistance is called insulators. |
| *    | Current can flow easily through conductors.                               | Current can not flow through insulators.                                    |
| *    | Copper, Iron etc.                                                         | Rubber, wood etc.                                                           |

4. State the precautions to be taken while using the electricity.

Ans - \* Electric switches & sockets should be fitted at a height at which small children cannot reach, put pins or nails inside. Pull a plug. wires should not be pulled while cleaning removing a plug from its socket.

\* Before cleaning an electrical appliances it should be switched off & its plug removed from the socket.

\* One's hands should be dry while handling an electrical appliance & as far as possible, one should use footwear with rubber soles. As rubber is an insulator, it prevents the current from flowing through our body.

thereby protecting it.

- \* If a person gets an electric shock, you should not touch that person. You should switch off the main switch & if the switch is too far or you do not know where it is located, then you should remove the plug from the socket if possible. If not then you should use a wooden pole to push that person away from the electric wire.

Q. Give Scientific reasons for:

- a. Connecting wires in a circuit are made up of copper & Aluminium.

Ans-\* Copper & Aluminium are metals having very low resistance.

- \* This helps the electric current to flow through them easily.

- \* Therefore copper & aluminium are used to make wires in a circuit.

- b. Wood & glass are good insulators.

Ans-\* Wood & glass have extremely high resistance.

\* The electric current cannot flow through them.

\* Therefore wood & glass are good insulators.

c. The materials used in fuse have a specific melting point.


Ans-\* Fuse wires are connected in series to the electrical appliances.

\* If for some reasons the current in the circuit increases excessively, the fuse wire gets heated up & melts.

\* The circuit gets broken & the flow of current stops, thus protecting the appliances.

Q89 Solve the following problem.


A. Find the resultant resistance:-

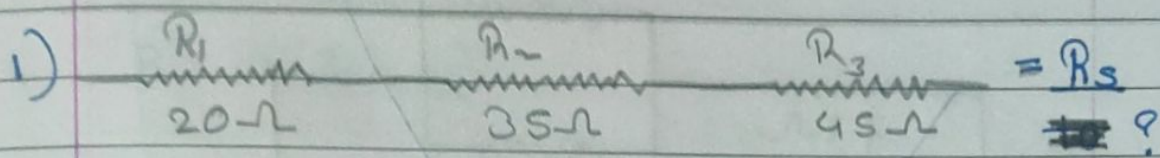

$\therefore R_1, R_2$  &  $R_3$  are connected in series  
 $\therefore$  the resultant resistance  $R_s$ ,

$$R_s = R_1 + R_2 + R_3 = 20\Omega + 35\Omega + 45\Omega$$

$\therefore R_s = 100\Omega$

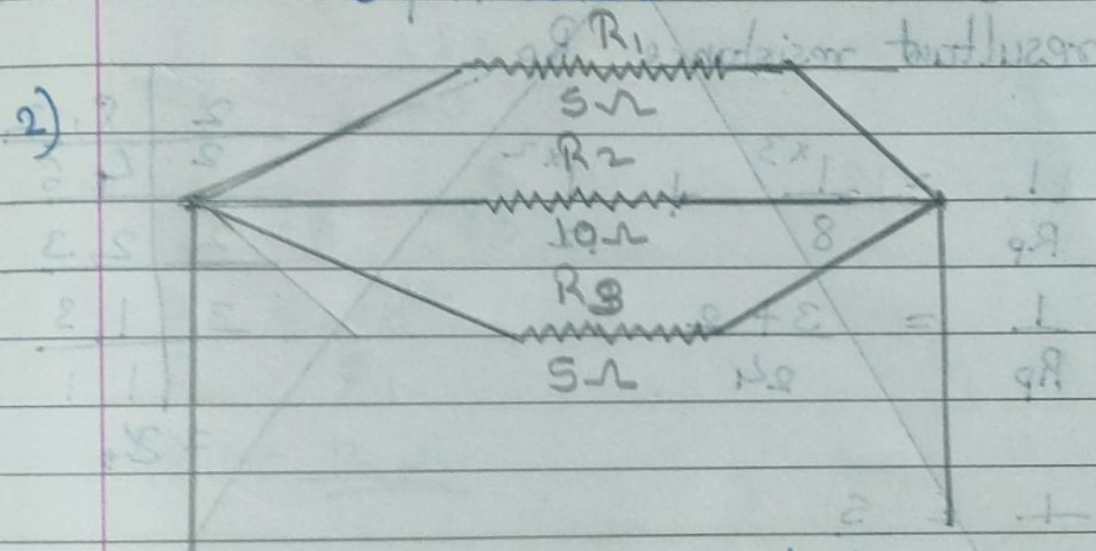

$\therefore R_1, R_2, R_3$  are connected in parallel

$$\therefore \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\therefore \frac{1}{R_p} = \frac{1}{5} + \frac{1}{10} + \frac{1}{5}$$

$$\therefore \frac{1}{R_p} = \frac{2 + 1 + 2}{10}$$

$$\therefore \frac{1}{R_p} = \frac{5}{10}$$

$$\therefore R_p = \frac{10}{5} = 2\Omega$$

|   |          |
|---|----------|
| 2 | 5, 10, 5 |
| 5 | 5, 5, 5  |
|   | 1, 1, 1  |
|   | = 10     |

3. Calculate the resultant resistance when the  
→ 2 resistance of  $20\ \Omega$  and  $30\ \Omega$  are connected  
in series and parallel  
→  $R_1 = 20\ \Omega$ ,  $R_2 = 30\ \Omega$

i) Series

$$R_s = R_1 + R_2 + R_3$$

$$R_s = 20 + 30$$

$$R_s = 50 \Omega$$

ii) Parallel

$$\frac{1}{R_P} = \frac{1}{20} + \frac{1}{30}$$


$$\frac{1}{R_P} = \frac{3+2}{60}$$

$$\frac{1}{R_P} = \frac{5}{60}$$

$$R_P = \frac{60}{5}$$

$$R_P = 12 \Omega$$

4.

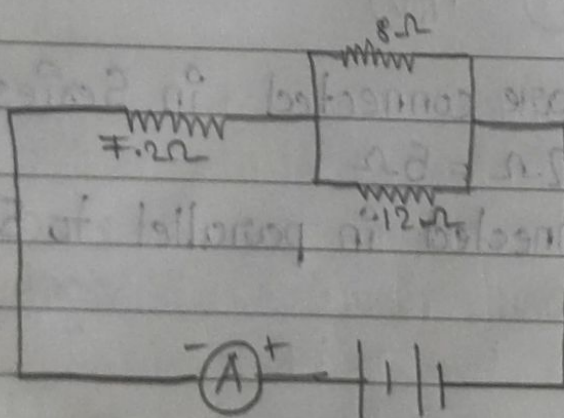

8  $\Omega$  & 12  $\Omega$  are connected  
 parallel  $\therefore$  the resultant resistance  
 $R_P$

$$\frac{1}{R_P} = \frac{1}{8} + \frac{1}{12}$$

$$\frac{1}{R_P} = \frac{3+2}{24}$$

$$\frac{1}{R_P} = \frac{5}{24}$$

$$R_P = 4.8 \Omega$$

$4.8\Omega$  &  $7.2\Omega$  are connected in Series


$\therefore$  The resultant resistance

$$= 4.8\Omega + 7.2\Omega$$

$$= 12.0\Omega$$

$$= 12\Omega$$

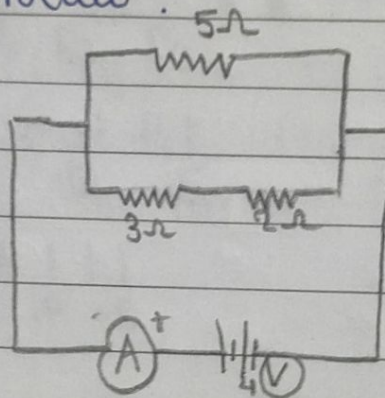5] Find the total  $\mathcal{I}$  &  $\mathcal{E}$  R in the given circuit.



$3\Omega$  and  $2\Omega$  are connected in Series

$$\therefore R_s = 3\Omega + 2\Omega = 5\Omega$$

$R_s = 5\Omega$  is connected in parallel to  $5\Omega$

$$\therefore \frac{1}{R_p} = \frac{1}{5} + \frac{1}{5}$$

$$\frac{1}{R_p} = \frac{1+1}{5}$$

$$\therefore \frac{1}{R_p} = \frac{2}{5}$$

$$\therefore R_p = \frac{5}{2}$$

$$\therefore R_p = 2.5\Omega$$

$$\frac{V}{\mathcal{I}} = R \text{ - ohm's law}$$

$$V = 4V, R = 2.5\Omega$$

$$\begin{array}{r} 1.6 \\ 5 \overline{) 8} \\ \underline{5} \\ 30 \\ \underline{30} \\ 0 \end{array}$$

$$\therefore I = \frac{V}{R} = \frac{4}{2.5} = \frac{4 \times 10^8}{255} = \underline{1.6A}$$

Q] A potential difference of ~~two hundred~~ (V) of 250 V is applied across a resistance (R) of 1000  $\Omega$  in an electric iron. Find the current (I) flowing through it?

Ans  $V = 250V$

$R = 1000\Omega$

$I = ?$

$\frac{V}{I} = R$  - ohms law

$$\therefore \frac{V}{R} = I$$

$$\frac{250}{1000} = I$$

$$\therefore I = \frac{1}{4}$$

$$\therefore \underline{0.25A}$$

b. When two resistors are connected in series, their effective resistance is  $80 \Omega$ . When they are connected in parallel, their effective resistance is  $20 \Omega$ . What are the values of the two resistors?

Ans. Let the two resistors be  $R_1$  &  $R_2$

$$R_1 + R_2 = 80$$

$$\therefore R_1 = 80 - R_2 \quad \text{--- (1)}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{20}$$

$$\frac{R_2 + R_1}{R_1 R_2} = \frac{1}{20}$$

$$\frac{R_2 + 80 - R_2}{(80 - R_2) R_2} = \frac{1}{20}$$

$$\frac{80}{80 R_2 - R_2^2} = \frac{1}{20}$$

$$(80 R_2 - R_2^2) = 80 \times 20 =$$

$$80 R_2 - R_2^2 = 1600$$

$$R_2^2 - 80 R_2 + 1600 = 0$$

$$R_2^2 - 40 R_2 - 40 R_2 + 1600 = 0$$

$$R_2(R_2 - 40) - 40(R_2 - 40) = 0$$

$$V(R_2 - 40)(R_2 - 40) = 0$$

$$R_2 - 40 = 0 \text{ or } R_2 = 40 \Omega$$

$$\therefore R_1 = 80 - 40$$

$$\therefore R_1 = 40 \Omega$$

$\therefore$  The two resistors are  $40 \Omega$  &  $40 \Omega$ .

(38)

Example I The resistance of the filament in a light bulb is  $1000 \Omega$ . If the bulb is fed by a current from a source of potential difference  $230 \text{ V}$ , how much current will flow through it?

Given:  $R = 1000 \Omega$

$V = 230 \text{ V}$

Formula:  $I = \frac{V}{R}$

$$\therefore I = \frac{230 \text{ V}}{1000 \Omega}$$

$$= 0.23 \text{ A}$$

$\therefore$  The current flowing through the filament of the bulb =  $0.23 \text{ A}$

Page No. 30  
Date: / /  
YOUVA

(35) Example 3: A current of ~~24~~ 0.24 A flows through a conductor when a potential difference of 24 V is applied between its two ends. What is its resistance?

Given:  $V = 24 \text{ V}$ ,  $I = 0.24 \text{ A}$

Formula:  $R = \frac{V}{I}$

$$\therefore I = \frac{24 \text{ V}}{0.24 \text{ A}}$$

for  $I = 0.24 \text{ A}$

$$R = 100 \Omega$$

The resistance of the conductor is  $100 \Omega$

(38) Example 4: Determine the current that will flow when a potential difference of 33 V is applied between two ends of an appliance having a resistance of  $110 \Omega$ . If the same current is to flow through an appliance having a resistance of  $500 \Omega$ , how much potential difference should be applied across its two ends.

Given:  $V = 30 \text{ V}$  &  $R = 110$

In the first case,  $A.C.D = \text{value}$

$$I = \frac{V}{R} = \frac{33}{110}$$

Current flowing through the applied force appliance  
 $= 0.3 \text{ A}$

In the second case  $2.15 = 0.2 = 98$

$$I = 0.3 \text{ A}, R = 500 \Omega$$

$$V = IR = 0.3 \times 500 \text{ V} = 150 \text{ V}$$

The required potential difference between its two ends = 150 V.

(40) Example: Three resistors having resistance of  $15 \Omega$ ,  $3 \Omega$  &  $4 \Omega$  are connected in series. What is the effective resistance in the circuit?

Given:  $R_1 = 15 \Omega$ ,  $R_2 = 3 \Omega$ ,  $R_3 = 4 \Omega$

$$\text{Effective resistance } R_s = R_1 + R_2 + R_3 = 15 + 3 + 4 = 22 \Omega$$

$\therefore$  The effective resistance in the circuit =  $22 \Omega$


(42) Example: Resistors having resistance of  $15 \Omega$ ,  $20 \Omega$  &  $10 \Omega$  are connected in parallel. What is the effective resistance in circuit?

Given:  $R_1 = 15 \Omega$ ,  $R_2 = 20 \Omega$  &  $R_3 = 10 \Omega$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{15} + \frac{1}{20} + \frac{1}{10} = \frac{4+3+6}{60} = \frac{13}{60}$$


Draw figures for the following

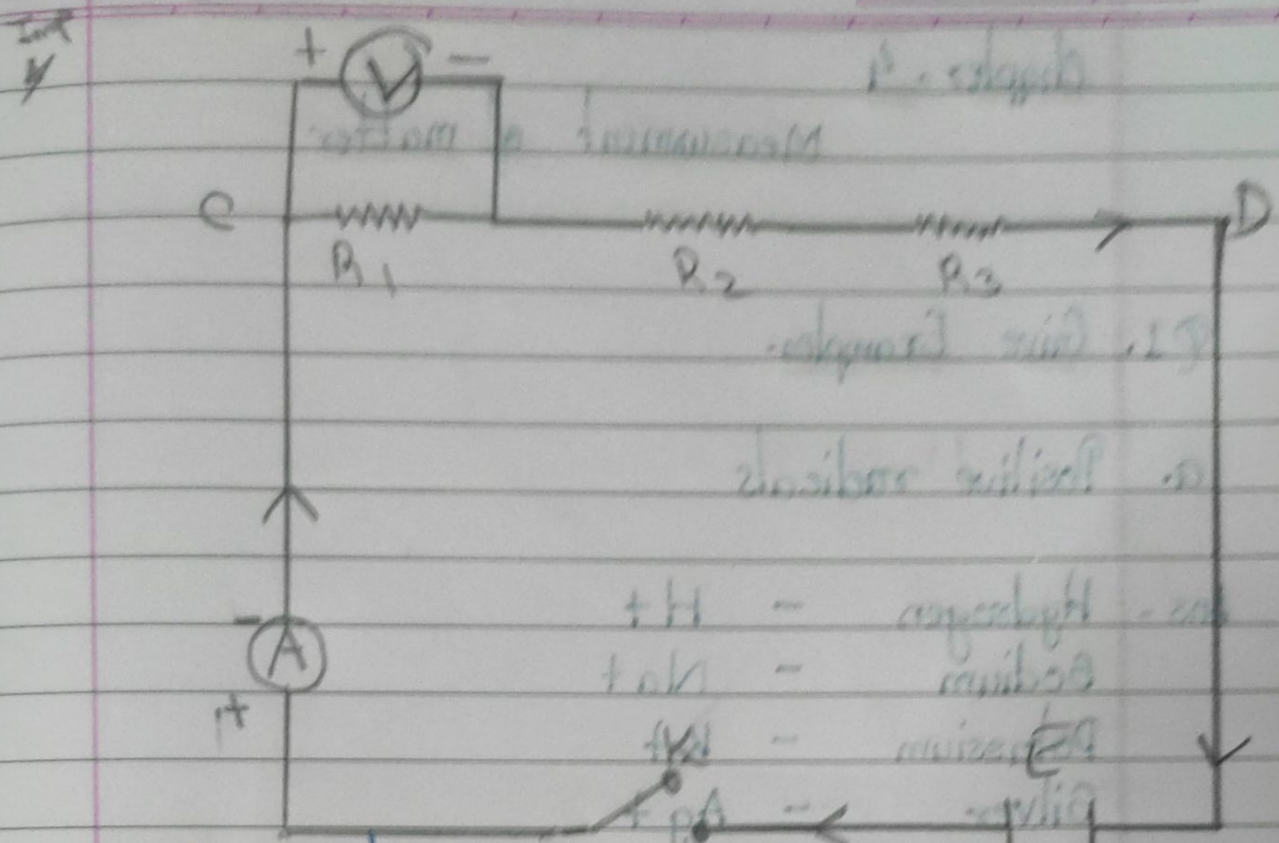

3.8 Resistor in Series

\*\* Imp

Resistor in Parallel

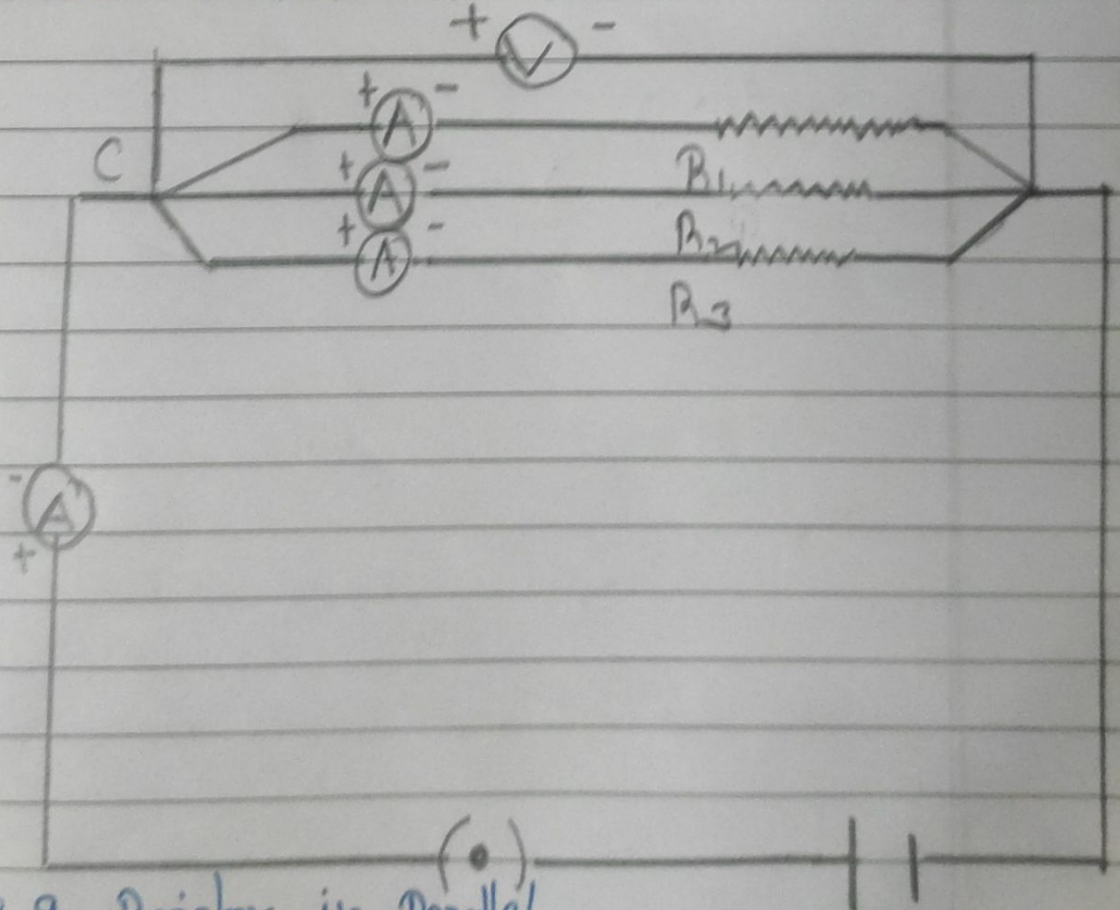

3.9 Resistor in Parallel.