

4) R ————
 R ————

If connected in series = $R + R = 2R$


If connected in Parallel = $\frac{1}{R} + \frac{1}{R} = \frac{2}{R}$

$$\frac{1}{R_p} = \frac{2}{R}$$

$$R_p = \frac{R}{2}$$

$$\frac{H_s}{H_p} = \frac{\frac{V^2}{R_s} \times T}{\frac{V_2}{R_p} \times T} = \frac{R_p}{R_s} = \frac{R}{2 \times 2R} = \frac{1}{4}$$

5)

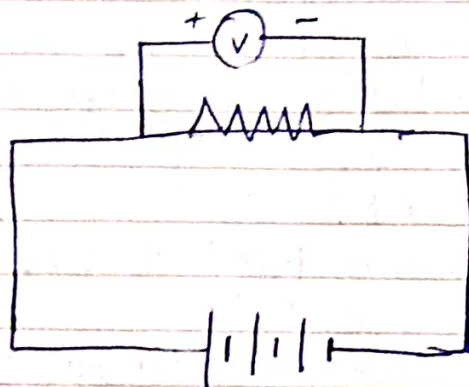

[Draw figure with pencil]

To Measure the Potential Difference between two Points, a Voltmeter should be connected in Parallel to the Points.

9) $R = 0.2 + 0.3 + 0.4 + 0.5 + 12 = 13.4 \Omega$

$$V = 9V$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{9}{13.4} = 0.671 A$$

10). $V = IR$

$$R = \frac{V}{I} = \frac{220}{5} = 44 \Omega$$

Total Resistance of wire is 44Ω

Let there be x No of 176Ω resistor

$$\frac{1}{R_p} = \frac{1}{176} \times x$$

$$R_p = \frac{176}{x}$$

$$44 = \frac{176}{x}$$

$$x = \frac{176}{44} = 4$$

11).


If the Resistance is connected in series, then the equivalent Resistance will be the sum of three resistance $= 6 + 6 + 6 = 18 \Omega$ which is not desired.

If we connect in parallel

$$\frac{6}{2} = 3 \Omega, \text{ which is not desired}$$

Hence we should connect two Resistance resistors in series or parallel


i) Two Resistor in Parallel

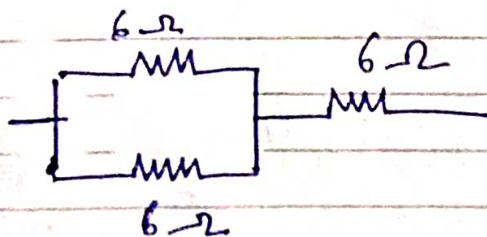

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{6} = \frac{1}{1+1} = 1 \times \frac{6}{2} = 3 \Omega$$

The Third 6Ω resistor is in Series with 3Ω
 Hence Equivalent Resistance in the Circuit
 $6\Omega + 3\Omega = 9\Omega$

11) Two Resistors in Series

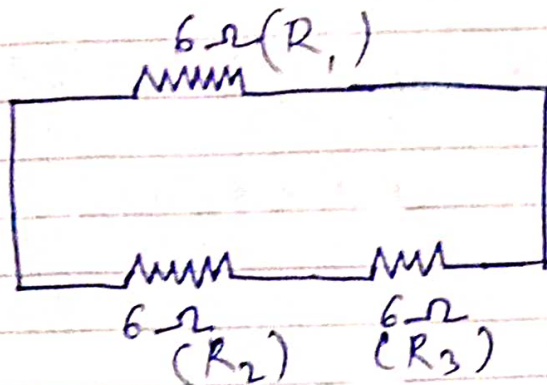

$$R_2 + R_3 = 6\Omega + 6\Omega = 12\Omega \quad [\text{Connected in series}]$$

$$R_2 + R_3 = R'$$

R_1 & R' are in Parallel $[12\Omega \text{ \& } 6\Omega]$

$$\frac{1}{\frac{1}{12} + \frac{1}{6}} = \frac{1}{\frac{1+2}{12}} = \frac{1 \times 12}{3} = 4\Omega$$

12). Resistance R_1 of the bulb is given by Expression

$$P_1 = \frac{(V_1)^2}{R_1}$$

$$R_1 = \frac{V^2}{P_1}$$

$$V = 220V$$

$$I = 5A$$

$$P_1 = 10W$$

$$R_1 = \frac{(220)^2}{10} = \frac{48400}{10} = 4840\Omega$$

According to ohm's Law

$$V = IR$$

R is the total Resistance of the Circuit for x number of Electric bulbs

$$R = \frac{V}{I} = \frac{220}{5} = 44 \Omega$$

Resistance of each Electric Bulb (R_1) = 4840Ω

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_1} + \dots \text{ up to } x \text{ times}$$

$$\frac{1}{R} = \frac{1}{R_1} \times n$$

$$n = \frac{R_1}{R} = \frac{4840}{44} = 110$$

Therefore, 110 Electric bulbs are Connected in Parallel.

37) $V = 220V$

$I = ?$

$R_A = 24 \Omega$


$R_B = 24 \Omega$



Separately



Series

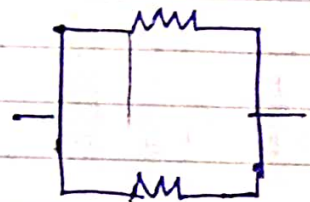

Parallel.

Case I When Connected Separately.

$$I_1 = \frac{V}{R_1} = \frac{220}{24} = 9.167 A$$

Case II When connected in Series

$$I_2 = \frac{V}{R_A + R_B} = \frac{220}{48} = 4.5835 A$$

Case III When Connected in Parallel.

$$I_3 = \frac{V}{R_A + R_B} = \frac{220}{12} = 18.33 A$$