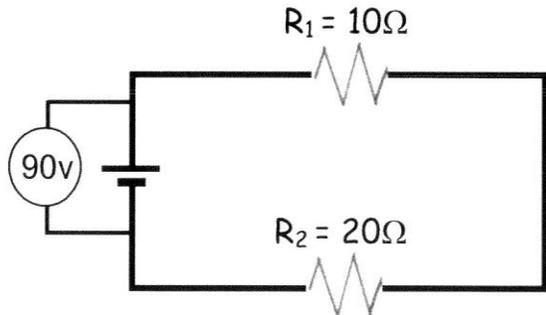



Worksheet- Series Circuit Problems, Episode 903 Name: _____

Remember: Series Circuit


- Current around the circuit does not change
- Voltage across each Resistor will have a Voltage Drop; Voltage Drops across ALL Resistors will ADD together to equal the Total Voltage
- Resistance: Add each resistor up to find Resistance Total i.e. $R_1 + R_2 + R_3 + \dots = R_T$



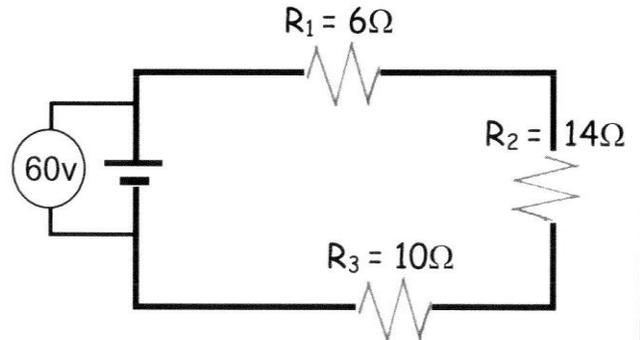
$R_T = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$



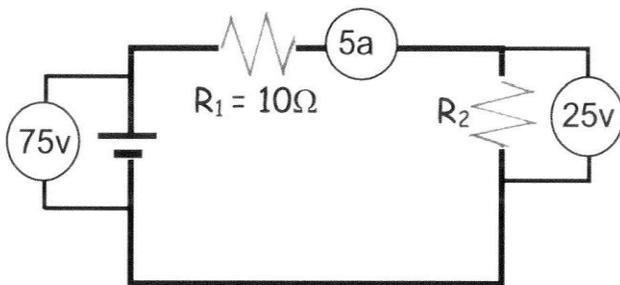
$R_T = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $I_3 = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $V_3 = \underline{\hspace{2cm}}$



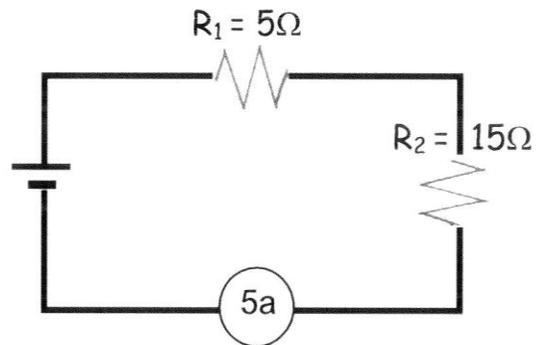
$V_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $R_2 = \underline{\hspace{2cm}}$



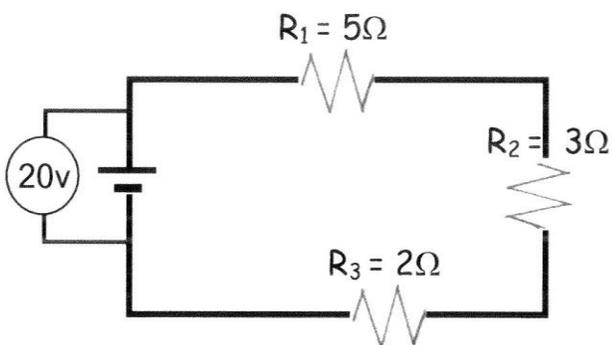$V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$



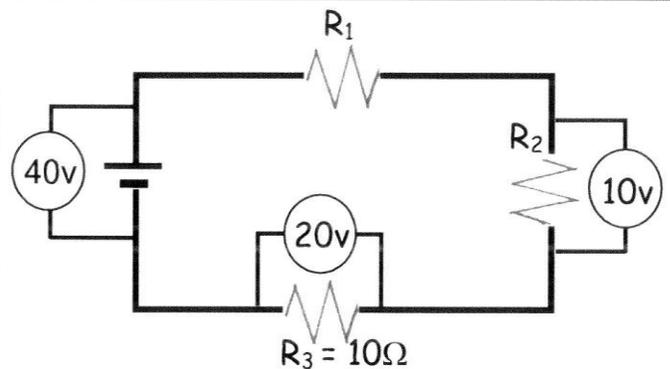
$R_T = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $V_3 = \underline{\hspace{2cm}}$




$I_3 = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $V_1 = \underline{\hspace{2cm}}$
 $R_1 = \underline{\hspace{2cm}}$ $R_2 = \underline{\hspace{2cm}}$

Remember: Parallel Circuit

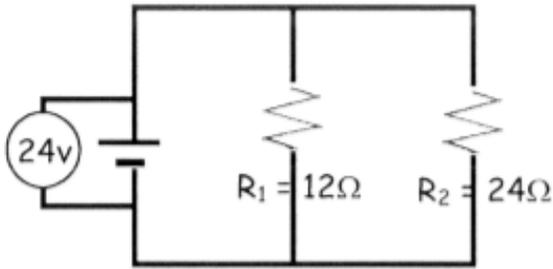
- Current in each branch will vary and will add up to the Total Amperage
- Voltage down each branch will be the same as the Total Voltage
- Resistance: $\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R_{EQ}}$ Find Inverse for Total Resistance = $\frac{R_{EQ}}{1}$



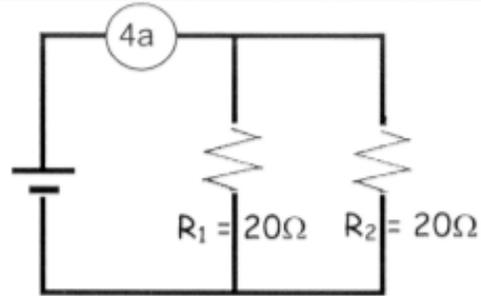
$R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_1 = \underline{\hspace{2cm}}$
 $V_2 = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$



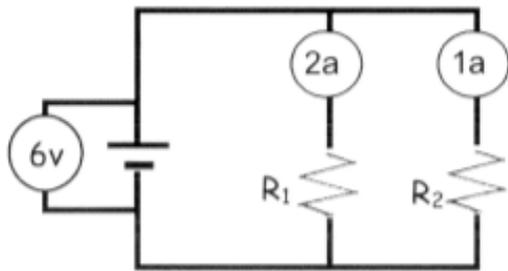
$R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$



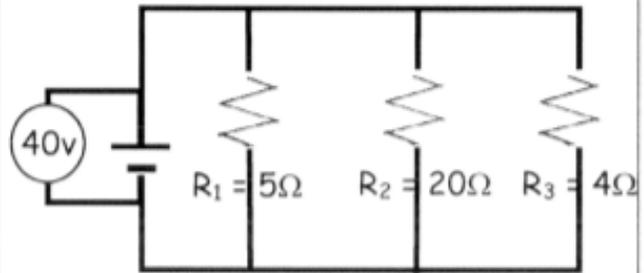
$V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$
 $R_1 = \underline{\hspace{2cm}}$ $R_2 = \underline{\hspace{2cm}}$ $R_{eq} = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$



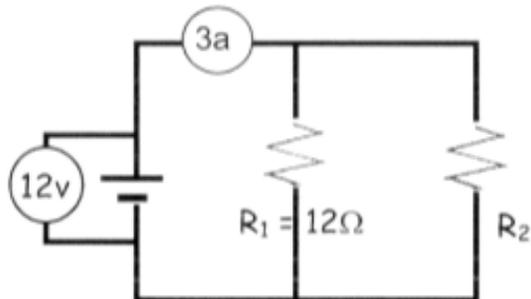
$R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $V_3 = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $I_3 = \underline{\hspace{2cm}}$



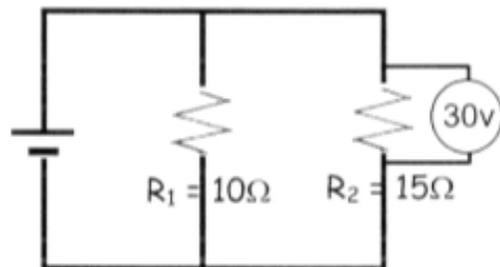
$V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$
 $I_T = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$
 $R_2 = \underline{\hspace{2cm}}$ $R_{eq} = \underline{\hspace{2cm}}$



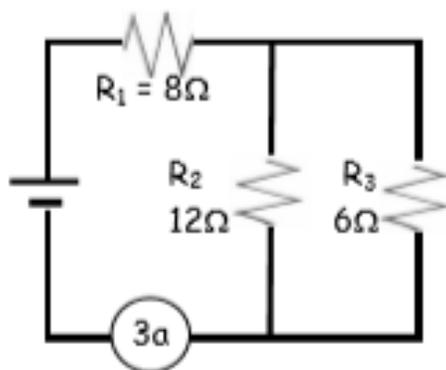
$V_1 = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$
 $R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$



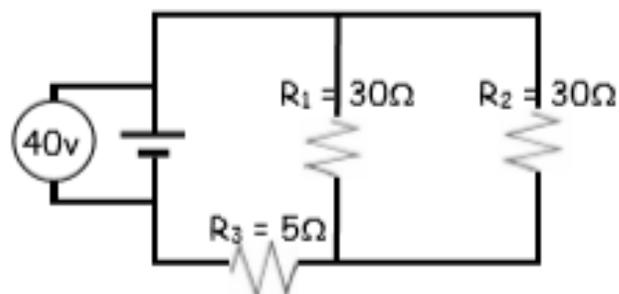
$R_T = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $V_3 = \underline{\hspace{2cm}}$



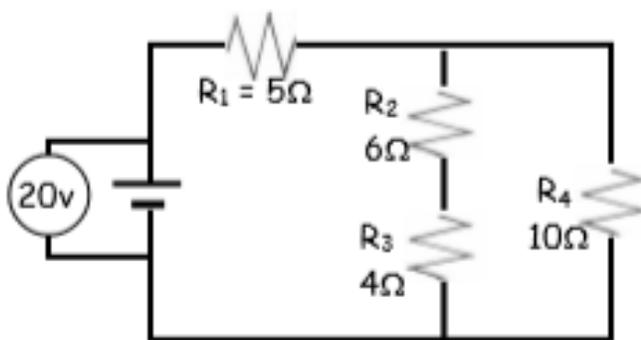
$R_T = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $I_3 = \underline{\hspace{2cm}}$
 $V_3 = \underline{\hspace{2cm}}$ $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$



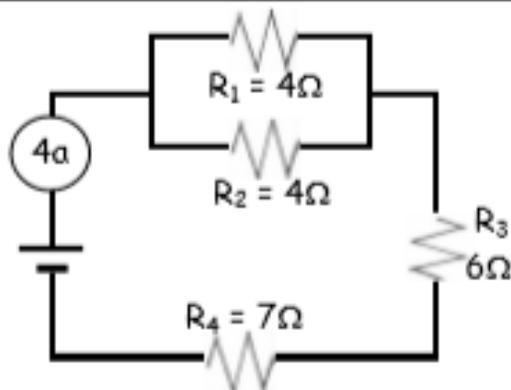
$R_T = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $V_4 = \underline{\hspace{2cm}}$ $I_4 = \underline{\hspace{2cm}}$



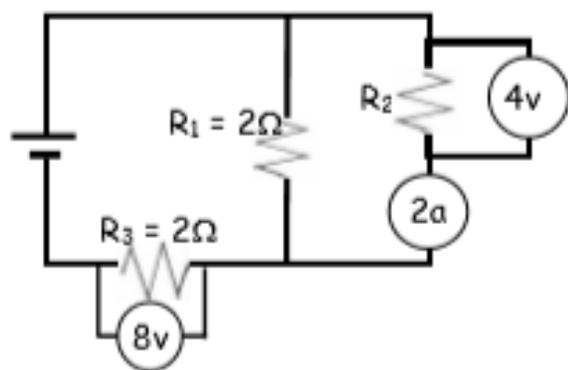$R_T = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $I_3 = \underline{\hspace{2cm}}$ $V_4 = \underline{\hspace{2cm}}$



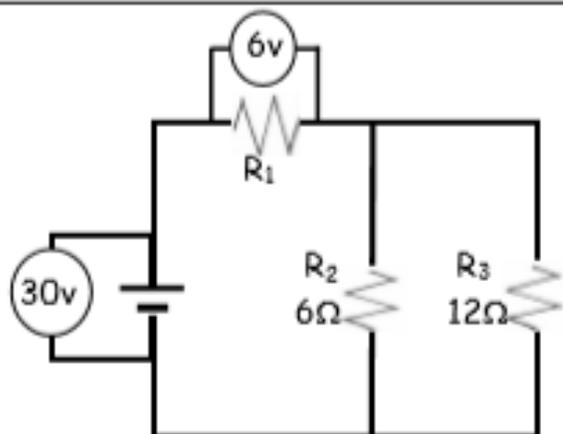$R_2 = \underline{\hspace{2cm}}$ $R_T = \underline{\hspace{2cm}}$
 $I_3 = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$
 $V_1 = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$



$V_2 = \underline{\hspace{2cm}}$ $V_3 = \underline{\hspace{2cm}}$
 $I_2 = \underline{\hspace{2cm}}$ $I_3 = \underline{\hspace{2cm}}$
 $I_1 = \underline{\hspace{2cm}}$ $R_1 = \underline{\hspace{2cm}}$ $R_T = \underline{\hspace{2cm}}$